

CSE232_2022_HW1

- 1) An autonomous car has a detector that measures the distances to the front car as a 4-bit binary number. 000 means very close, 111 means long enough. (50 points)
 - a) Create a circuit that turns on breaks when the distance is below 2, turn on the yellow led if the distance is between 3 to 10 and turn on the green led if the distance is higher than 11.
 - b) Express the functions on a) by using sum of minterms and product of maxterms.

Hint: You are expected to get three outputs at your circuit.

- 2) Prove that $(a+c)(a+b')(b+c) = (a+b')(b+c)$ by using Boolean Algebra (30 points)
- 3) Draw the circuit of $F = A'BD + CD$ using only two input NAND gates (20 Points)

Deadline: 10.03.2022 23:59